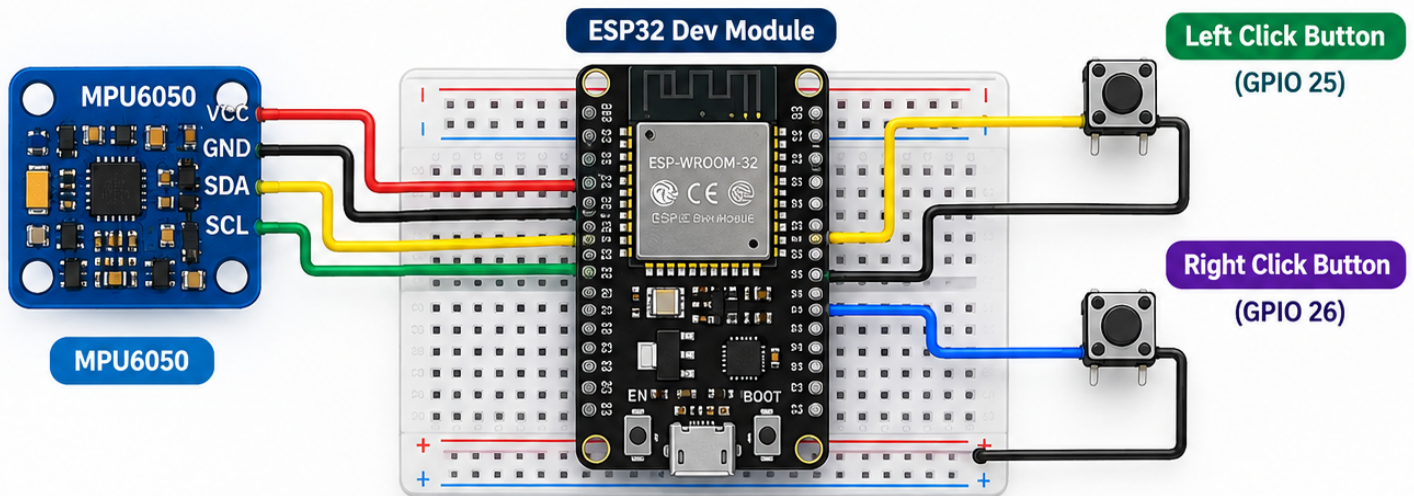




ESP32 Wireless Mouse – Circuit Diagram

MPU6050 + 2 Buttons | Bluetooth HID | No Receiver Required



Wiring Table

MPU6050 → ESP32 (I2C)

MPU6050 Pin	ESP32 Pin
VCC	3.3V
GND	GND
SDA	GPIO 21
SCL	GPIO 22

Push Buttons

Function	ESP32 Pin	Other Terminal
Left Click	GPIO 25	GND
Right Click	GPIO 26	GND

ESP32 Pin Summary

GPIO 21	→ SDA (MPU6050)
GPIO 22	→ SCL (MPU6050)
GPIO 25	→ Left Button
GPIO 26	→ Right Button
3.3V	→ MPU6050 VCC
GND	→ MPU6050 GND & Buttons

Components Used

ESP32 Development Board	× 1
MPU6050	× 1
Push Button	× 2
Breadboard	× 1
Jumper Wires	× As required
USB Cable	× 1



Important Notes

- Use 3.3V for MPU6050 (not 5V).
- Use `INPUT_PULLUP` for buttons.
- Button pressed = LOW.
- Common GND for all components.
- Ensure proper wiring and check pin numbers.

Wiring Complete!

Now upload the code, pair with your computer, and start using your ESP32 Wireless Mouse!

Build + Learn + Create

Small Project – Big Ideas